



ABES Engineering College, Ghaziabad
Department of Applied sciences & Humanities

Session: 2025-26




Semester: II






Section:



Course Code: 25EL201

Course Name: Basics of Electrical Engineering

Assignment Sheet-1 (Unit-1)

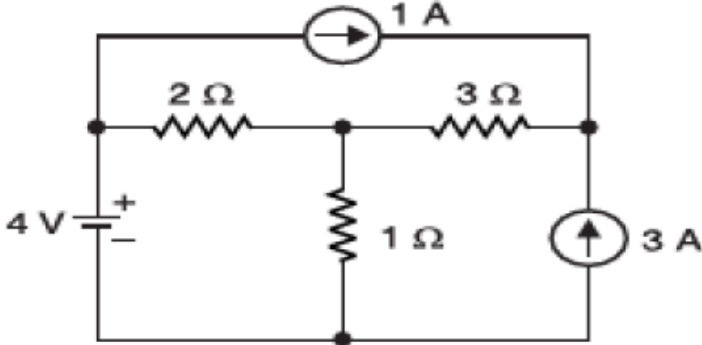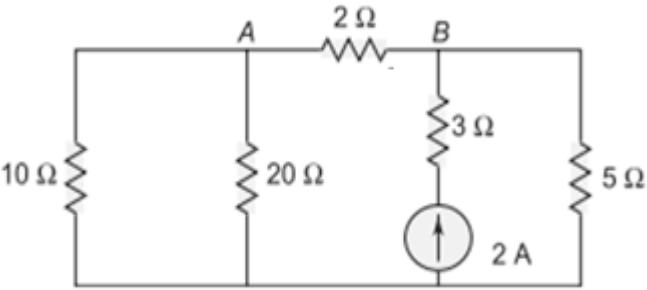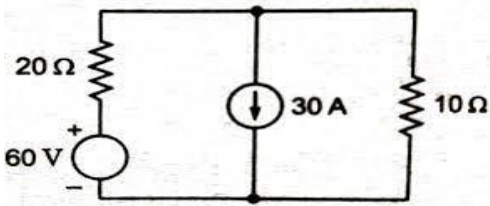Q. No.	KL	CO	Question	Ans.
Q-1	K3	CO1	Using Mesh analysis, find current in $1\ \Omega$ resistor in the circuit shown in figure and verify answer by using Nodal analysis and Superposition theorem. 	$I_{1\Omega} = 4A$
Q-2	K3	CO1	Calculate the current in $2\ \Omega$ by using mesh analysis and verify answer by using Nodal and Thevenin's theorem 	$I_{2\Omega} = 0.731A$
Q-3	K3	CO1	Calculate the current in $10\ \Omega$ by using Mesh analysis, Nodal, analysis Superposition, Thevenin and Norton's Theorem. 	$I_{10\Omega} = 18A$

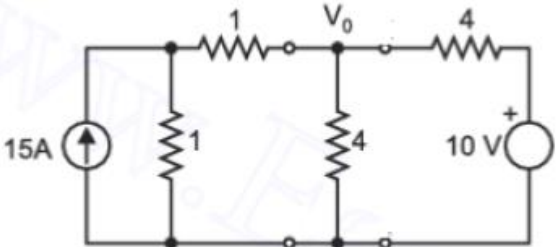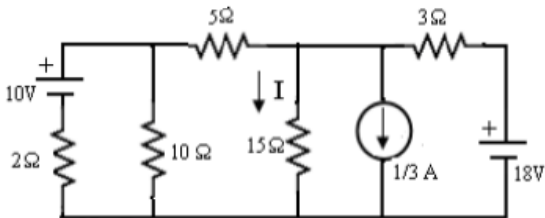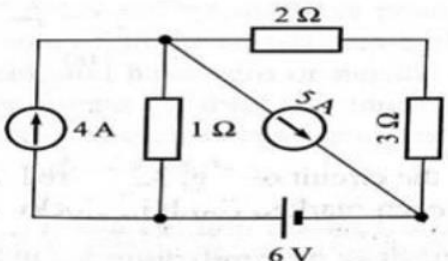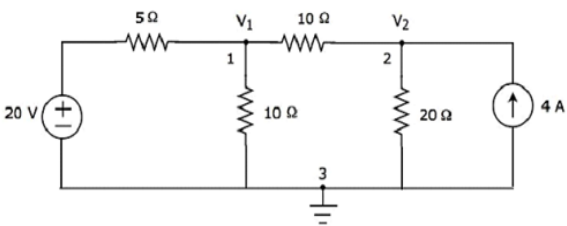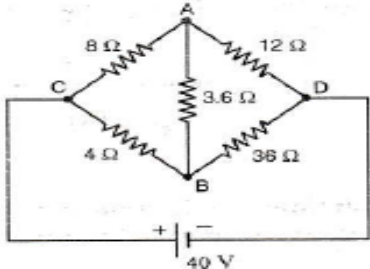Q-4	K3	CO1	Determine the Voltage V_o in the given Circuit by Mesh, Nodal and Superposition theorem. 	$V_o = 10 \text{ V}$
Q-5	K3	CO1	Determine Current I by using Nodal analysis 	$I = 0.838 \text{ A}$
Q-6	K3	CO1	Determine Voltage drop in 3Ω Resistor Using Mesh and Nodal Analysis. 	$V = 2.5 \text{ V}$
Q-7	K3	CO1	Calculate the current in 20Ω by using Mesh analysis, Nodal, analysis Superposition, Thevenin and Norton's Theorem. 	$I_{20\Omega} = 2 \text{ A}$
Q-8	K3	CO1	Calculate the current in AB branch by using Mesh analysis, Nodal, analysis, Thevenin and Norton's Theorem 	$I_{AB} = 1 \text{ A} \text{ B to A}$

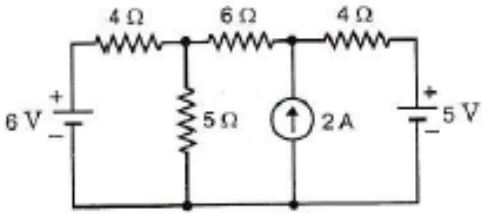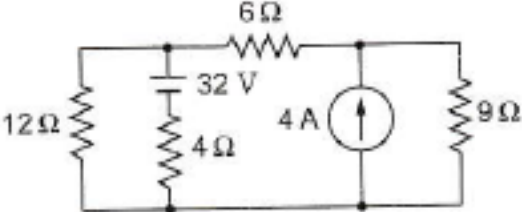Q-9	K3	CO1	Determine current in 6Ω resistance using source transformation. 	$I_{6\Omega} = 0.79\text{A}$
Q-10	K3	CO1	Calculate the current in 6Ω by using Mesh, Nodal analysis, Superposition, Thevenin and Norton's Theorem. 	$I_{6\Omega} = 0.667\text{ A}$